

Computer Science 03 – 60 – 265 – 01
Second Midterm Examination
Tuesday, June 15th 2004

Dr. Alioune Ngom

Last Name:

First Name:

Student Number:

INSTRUCTIONS

- EXAM DURATION IS 90 MINUTES.
- CALCULATORS, NOTES AND BOOKS ARE NOT ALLOWED.
- CHEATING IS NOT ALLOWED AND I WILL GIVE 0 FOR CHEATING.
- READ ALL QUESTIONS CAREFULLY BEFORE ANSWERING.
- WRITE YOUR FINAL ANSWERS IN THE FRONT OF PAGES. USE THE BACK OF PAGES FOR SCRAP WORKS.
- **WRITE YOUR FINAL ANSWERS WITH A PEN.**
- Attempt all questions.
- If you need to make any assumptions, state them clearly with your answers.
- Write your answer neatly. Messy work is very hard to read and may cause you to lose marks.
- Lists of Boolean properties and logic gates are given on pages 19 and 20.

Questions	Q#1	Q#2	Q#3	Total
Marks				
Totals	20	10	20	100

Question #1: (20 points) The following is the specification of a circuit that has four inputs called a, b, c, d , and four outputs called w, x, y, z . The inputs represent the *valid* BCD code of a decimal digit. The function of the circuit is to generate the Excess-3 code of the 9's complement of the input digit. The 9's complement \bar{D} of a decimal digit D is defined as $\bar{D} = 9 - D$ (for instance, $\bar{3} = 6$, $\bar{7} = 2$, $\bar{0} = 9$, $\bar{5} = 4$, ...).

- Fill in the truth table below that shows the four outputs

a	b	c	d	w	x	y	z
0	0	0	0				
0	0	0	1				
0	0	1	0				
0	0	1	1				
0	1	0	0				
0	1	0	1				
0	1	1	0				
0	1	1	1				
1	0	0	0				
1	0	0	1				
1	0	1	0				
1	0	1	1				
1	1	0	0				
1	1	0	1				
1	1	1	0				
1	1	1	1				

K-map for w

K-map for x

K-map for y

K-map for z

K-map for \bar{w}

K-map for \bar{x}

K-map for \bar{y}

K-map for \bar{z}

For each question on page 3, fill in the corresponding K-map above, accordingly.

2. Derive the minimal SOP expressions for w and x .

$$w = \dots$$

$$x = \dots$$

3. Derive the minimal POS expressions for y and z .

$$y = \dots$$

$$z = \dots$$

4. Derive the minimal POS expressions for

- \bar{w} by the *Direct Method*.

$$\bar{w} = \dots$$

- \bar{x} by the *Complement Method*.

$$\bar{x} = \dots$$

5. Derive the minimal SOP expressions for

- \bar{y} by the *Direct Method*.

$$\bar{y} = \dots$$

- \bar{z} by the *Complement Method*.

$$\bar{z} = \dots$$

Space for rough work for Question #1

Space for rough work for Question #1

Question #2: (10 points) The circuit shown below has the output f and the inputs x and y . You must show all of the steps for the questions below.

1. Derive the logic expressions for the intermediate nodes A, B, C and the output f (do not minimize f).

$$A =$$

$$B =$$

$$C =$$

$$f =$$

Question #3: (20 points) Design a Full Subtractor

Space for rough work for Question #3

Space for rough work for Question #3

